

# **TEMPERATURE CONTROLLED FAN**


# Overview

- Introduction
- Block Diagram
- Hardware Requirements
- Software used
- Applications
- Future Work
- References

# Introduction

- Temperature controller controls the temperature of any device according to its requirement.
- Temperature sensor is interfaced to analog pin of Arduino board.
- Pulse Width Modulation(PWM) output is fed to a DC Fan through a motor driver IC.
- Liquid Crystal Display(LCD) displays the temperature of the device.
- The fan speed is proportional to the temperature measured.

# Block Diagram

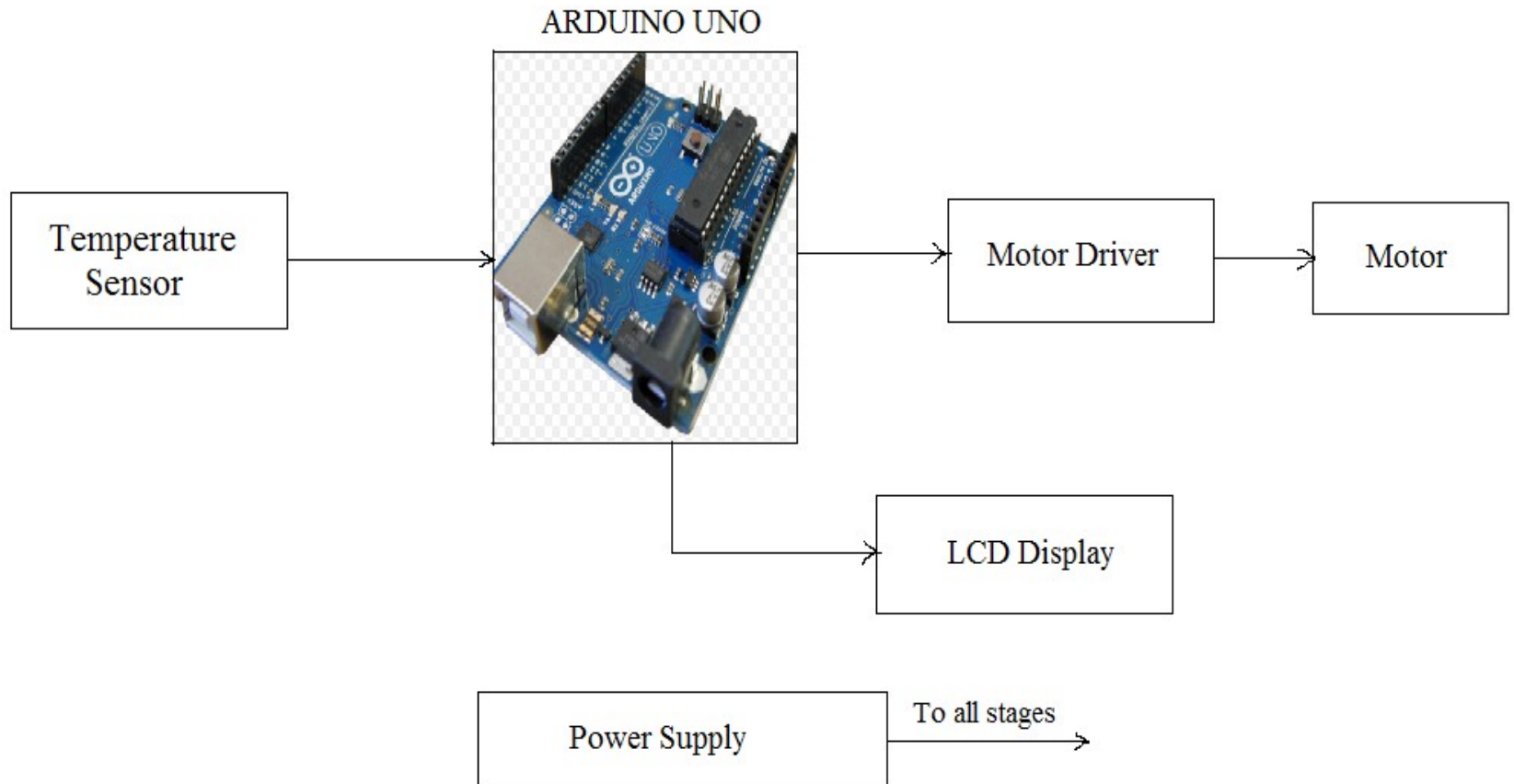


# Hardware requirements

- Arduino UNO
- Temperature Sensor-LM35
- DC Motor Driver-L293D
- DC Motor
- Power Supply

# Arduino UNO

- The Arduino Uno is a microcontroller board based on the ATmega328P.
- 14 digital input/output pins (of which 6 can be used as PWM outputs)
- 6 analog inputs.
- 16 MHz quartz crystal
- A power jack
- Connect it to a computer with a USB cable or power it with a AC-to-DC adapter or battery to get started.


# The board...

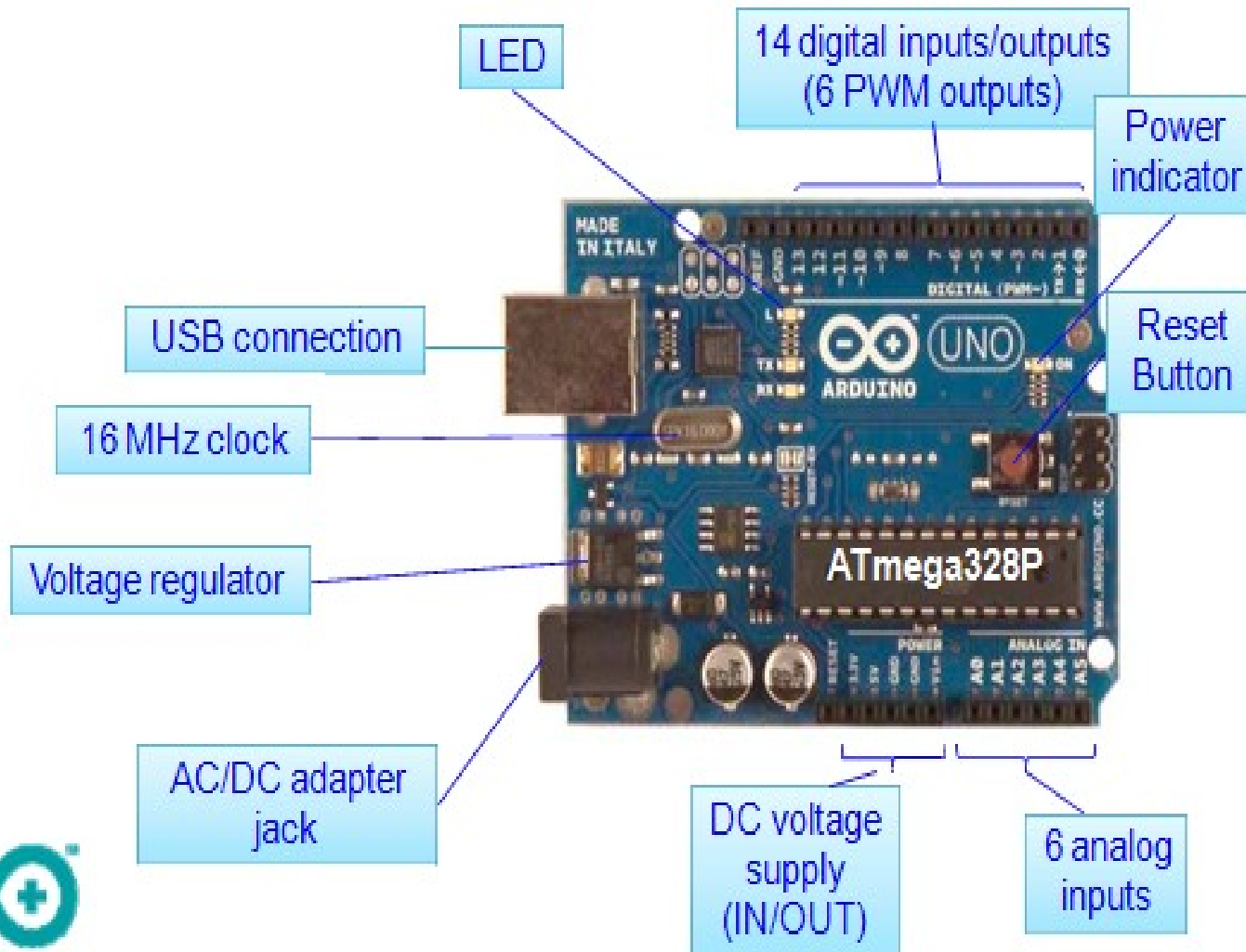






# Pin Diagram

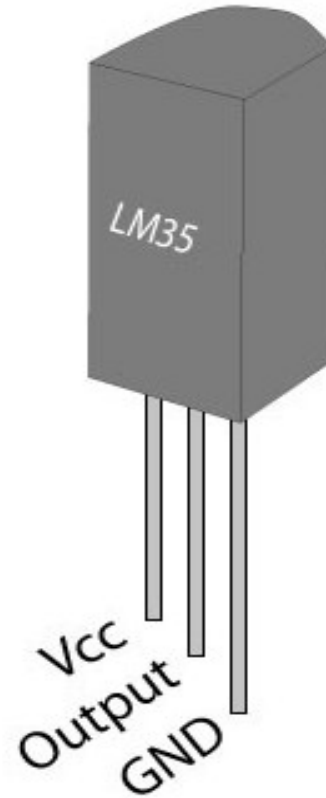


- LM35 digital sensor has got 3 pins VCC, GND and output pin.
- when it is heated the voltage at output pin increases, it is connected to the analog to digital convertor IC (ADC).
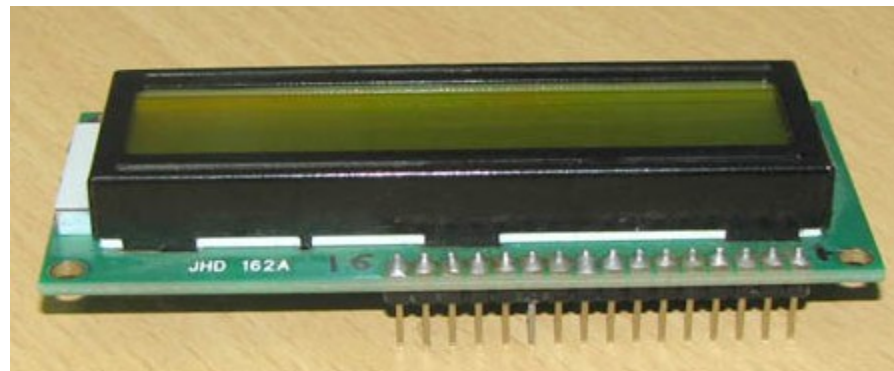
## Liquid Crystal Display (LCD)

- LCD screen is an electronic display module.
- Most common LCDs connected to the microcontrollers are 16x2 and 20x2 displays.
- A 16x2 LCD means it can display 16 characters per line and there are 2 such lines.
- Each character is displayed in 5x7 pixel matrix.
- 16x2 LCD has two registers, Command and Data.



# Pin Diagram

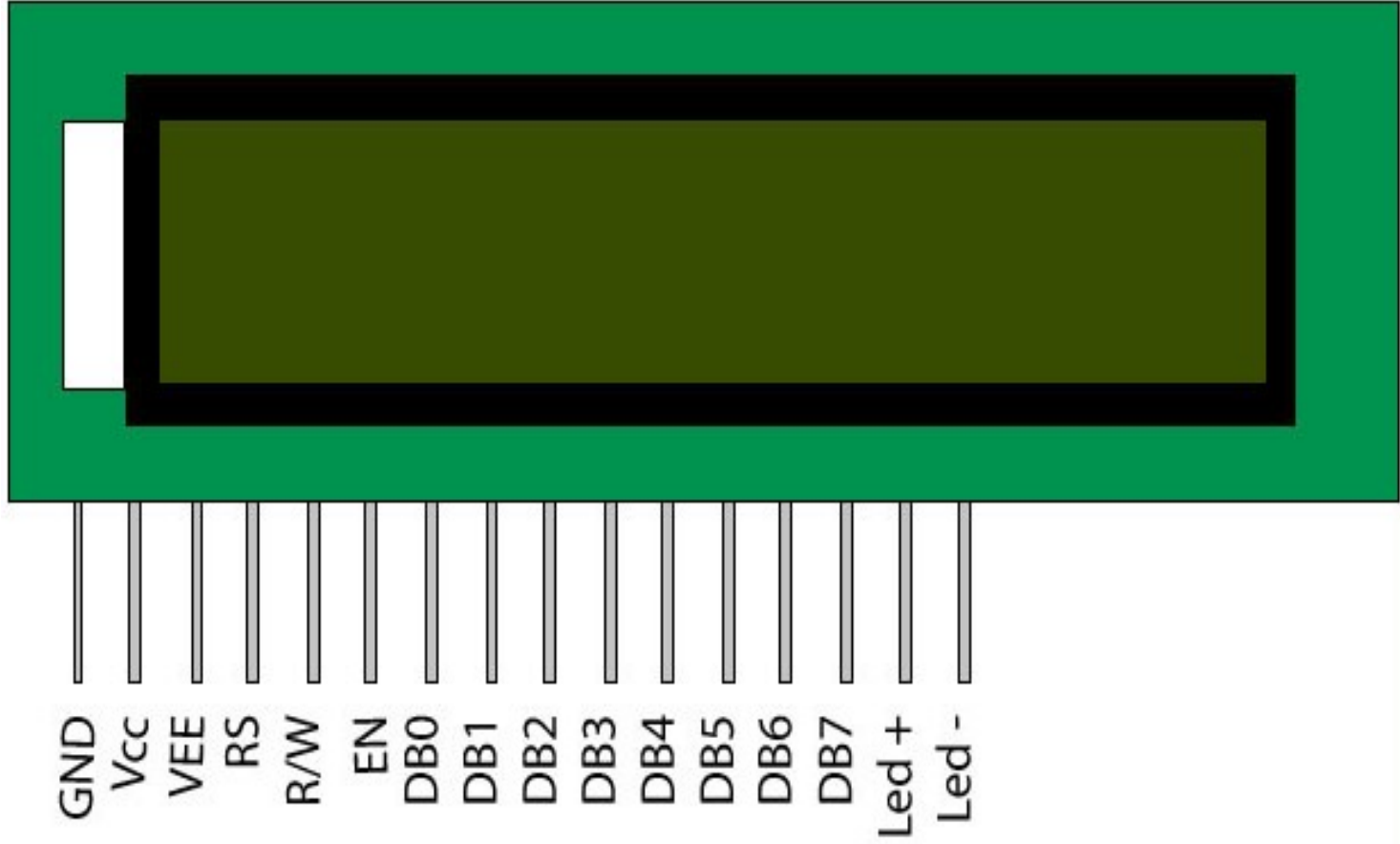


# Why LCD??

- LCDs are,
  - economical
  - easily programmable
  - have no limitation of displaying
- In this module it displays the temperature of the device.


# DC Motor Driver(L293D)

- L293D has quadruple high current half-H drivers.
- Wide Supply-Voltage Range: 4.5 V to 36 V
- High-Noise-Immunity Inputs
- Output Current 600mA Per Channel
- Peak Output Current 1.2A Per Channel.

# Pin Diagram

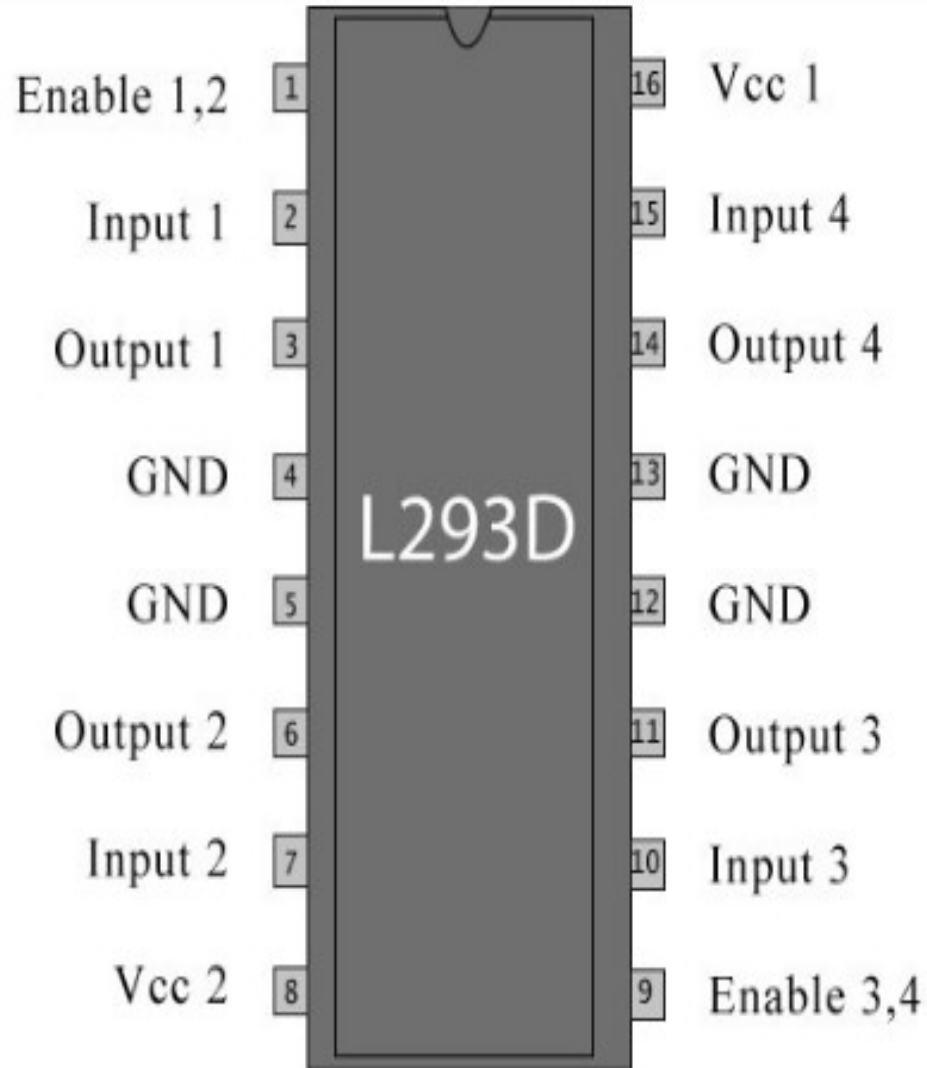


# Circuit Diagram

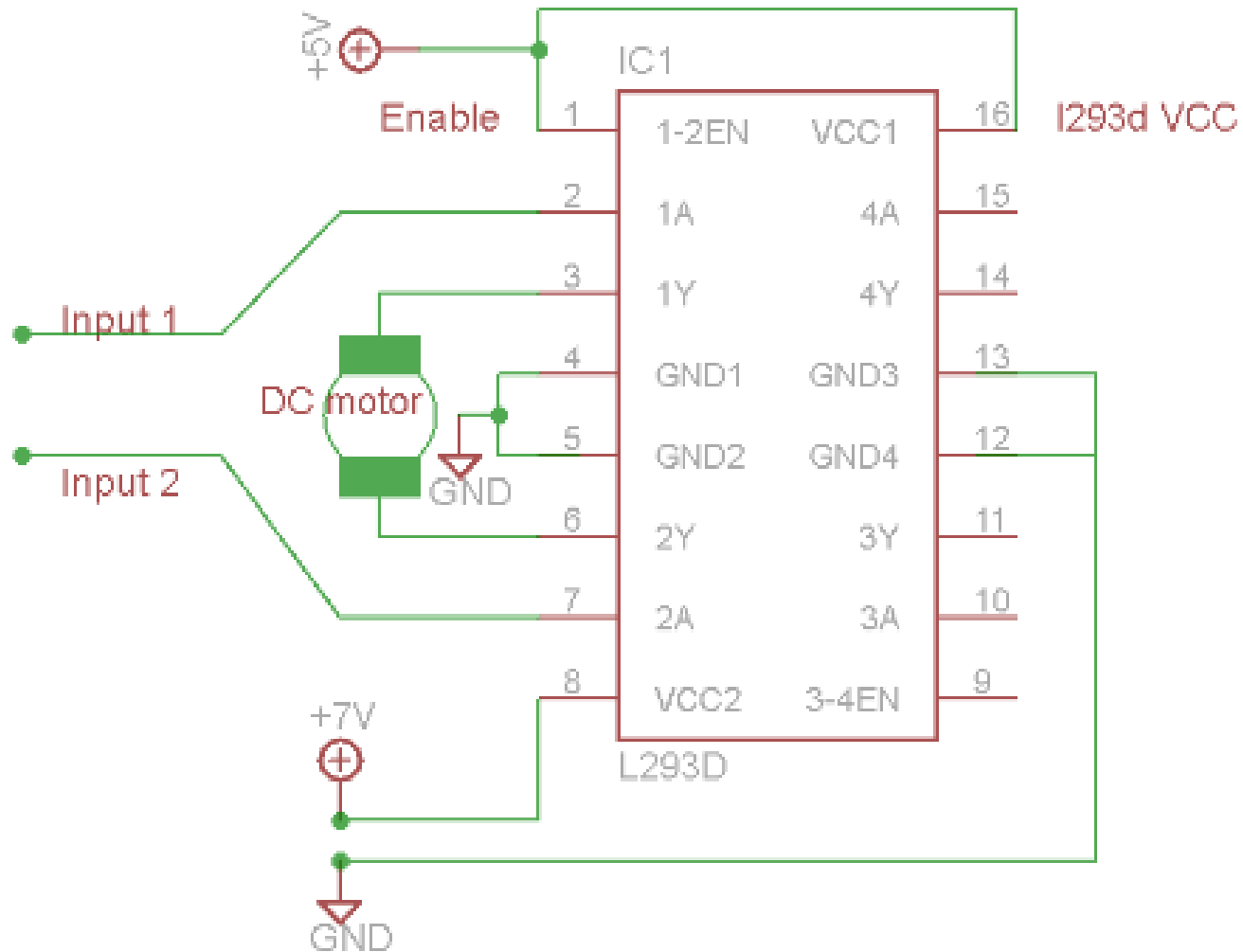


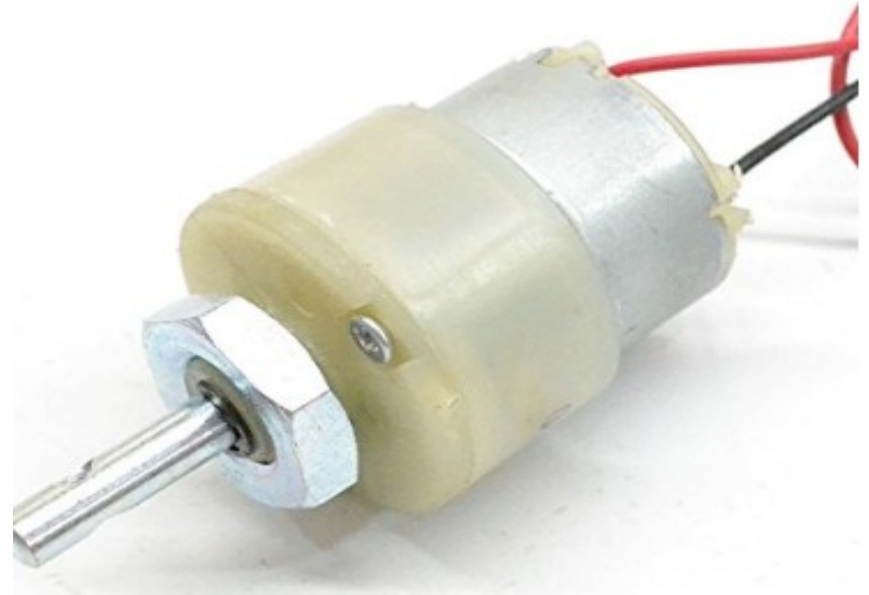
# DC Motor

- 10 to 200RPM 12V DC motors with Gearbox
- 6mm shaft diameter with internal hole
- No-Load Current=60mA(max)
- Load Current=300mA(max)





# Power Supply

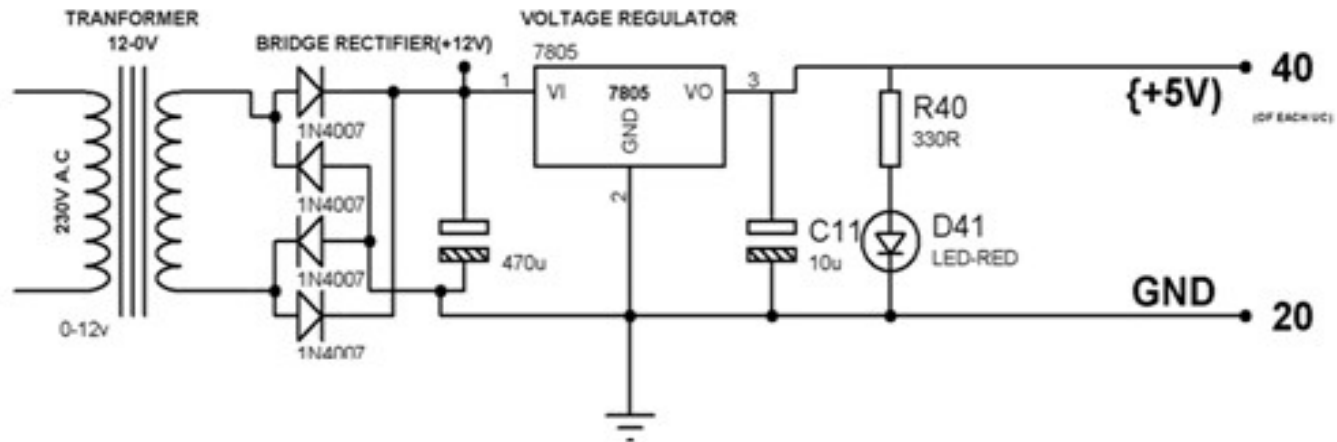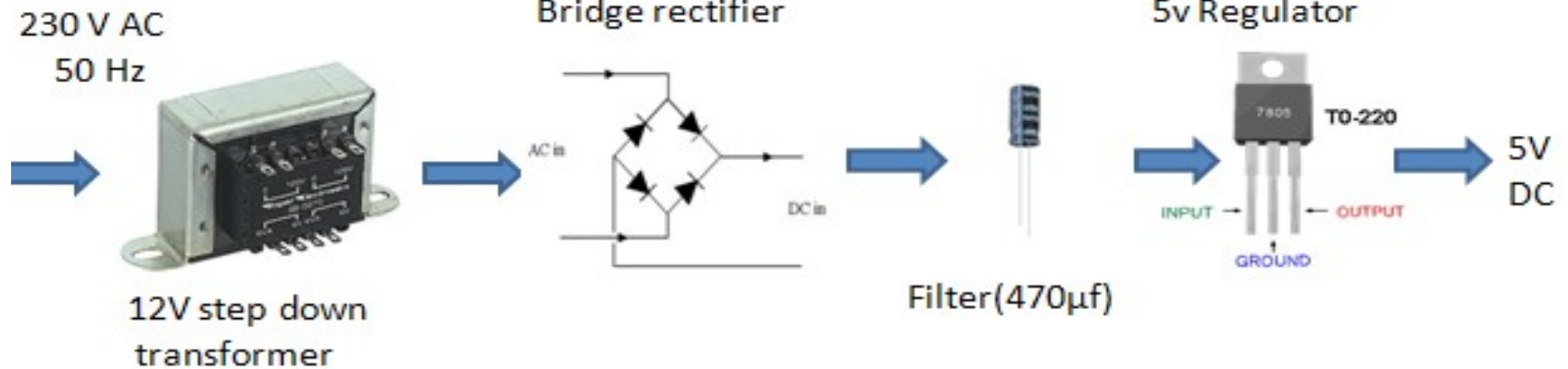

# Software Used

- Arduino IDE

## Programming Languages Used

- Embedded C/C++

# Applications

- This module can be used everywhere where power consumption has to be controlled
- It can be use to cool the processor in computers.

# Future Work

- This concept can be utilized further by interfacing it with more device like Air conditioner.
- User-defined temperature settings can be done using push buttons provided through Arduino board.

# References

- [www.atmel.com](http://www.atmel.com)
- [www.arduino.org](http://www.arduino.org)
- [www.beyondlogic.org](http://www.beyondlogic.org)
- [www.wikipedia.org](http://www.wikipedia.org)
- [www.elementzonline.com](http://www.elementzonline.com)
- [www.elementztechblog.wordpress.com](http://www.elementztechblog.wordpress.com)

**Questions????**

**THANK YOU**